

# I - ASSIGNMENT

(Start Writing From Here)

- 1) Convert the following decimal numbers to the indicated bases.

a)  $7562.45$  to octal.

first consider the integral part and divide it with 8.

$$\begin{array}{r} 8 | 7562 \\ 8 | 945 \quad 2 \\ 8 | 118 \quad -1 \\ 8 | 14 \quad -6 \\ \quad \quad 1 \quad -6 \end{array}$$

$\therefore$  The binary number of  $7562$  is  $16612$ .

Now, consider the decimal part, i.e.,  $0.45$ .

and multiply the number with 8.

$$\Rightarrow 0.45 \times 8 = 3.60$$

$\Rightarrow$  [Consider the part after the decimal part and multiply it with 8]

$$\Rightarrow 0.60 \times 8 = 4.8$$

$$\Rightarrow 0.8 \times 8 = 6.4$$

$$\Rightarrow 0.4 \times 8 = 3.2$$

$$\Rightarrow 0.2 \times 8 = 1.6$$

[so, now we have to do the same process until we get zero].

(3)

CMRIT

But for some problems we get a lengthy and long solution. So we can consider upto 4-5 digits.

Consider the decimal before digit from the order, up to down that means top to bottom.

$$\Rightarrow \begin{array}{r} 3.60 \\ 4.8 \\ 6.4 \\ 3.2 \\ 6.6 \end{array}$$

Consider these values and combine it with the binary Number.

$$\Rightarrow \text{Binary number} = 1661_2$$

$\therefore 7562.45$  into octal format is;  
 $(16612.3463)_8$

(b)  $1938.257$  to hexadecimal.

Step ① :- Separate the given number and write binary number for decimal part <sup>hexadecimal</sup> i.e.,

$1938 \rightarrow$  into bit hexadecimal

that means, divide the number with 16.

$$\begin{array}{r} 16 \mid 1938 \\ 16 \quad \boxed{121-2} \\ \quad \boxed{7-9} \end{array}$$

$\therefore$  The hexadecimal number of 1938 is  
792<sub>16</sub>

Step-(2):-

Consider the floating point and multiply it with 16.

$$\Rightarrow 0.257 \times 16 = 4.112$$

$$\Rightarrow 0.112 \times 16 = 1.792$$

$$\Rightarrow 0.792 \times 16 = 12.672$$

$$\Rightarrow 0.672 \times 16 = 10.752$$

[ $\because$  we can write, 12 as  $\rightarrow C$  and 10 as  $\rightarrow D$ ].

So, the final answer is

$$(792.41CA)_{16}$$

$\therefore$  1938.257 into hexadecimal is

$$(792.41CA)_{16}$$

(C) 175.175 to binary.

Step-(1):-

Consider the decimal part and convert the number into binary. i.e., converting 175 into binary by multiplying with 2.

$$\begin{array}{r}
 2 | 175 \\
 2 | 87 - 1 \\
 2 | 43 - 1 \\
 2 | 21 - 1 \Rightarrow (1010111)_2 = 175 \\
 2 | 10 - 1 \\
 2 | 5 - 0 \\
 2 | 2 - 1 \\
 1 - 0
 \end{array}$$

Step-(a):- Consider the floating point & multiply with 2.

$$\begin{aligned}
 \Rightarrow 0.175 \times 2 &= 0.35 \\
 0.35 \times 2 &= 0.7 \\
 0.7 \times 2 &= 1.4 \\
 0.4 \times 2 &= 0.8 \\
 0.8 \times 2 &= 1.6
 \end{aligned}$$

Now combine the floating point & decimal part numbers.

$$=(1010111.00101)_2$$

$\therefore 175.175$  into binary is

$$\rightarrow (1010111.00101)_2 //$$

② State and prove De-Morgan's theorem 1<sup>st</sup> and 2<sup>nd</sup> with logic gates and truth table.

→ Here, we have two theorems in De-Morgan's theorem.

The first one is  $\overline{AB} = A' + B'$

The second one is  $\overline{A+B} = \overline{A} \cdot \overline{B}$


Let us consider the first one,

(i)  $\overline{AB} = A' + B'$


The complement of a logical product equals the logical sum of complements.

Logic Gates

LHS :-

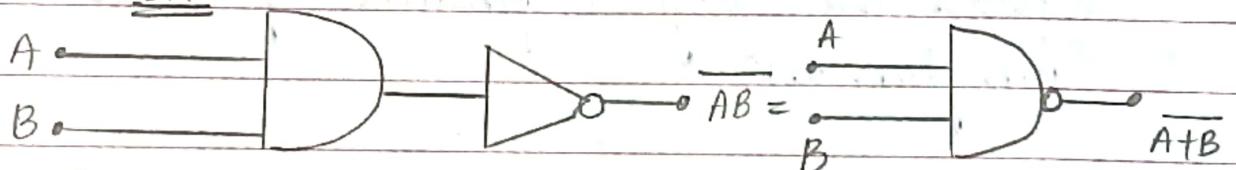

RHS :-

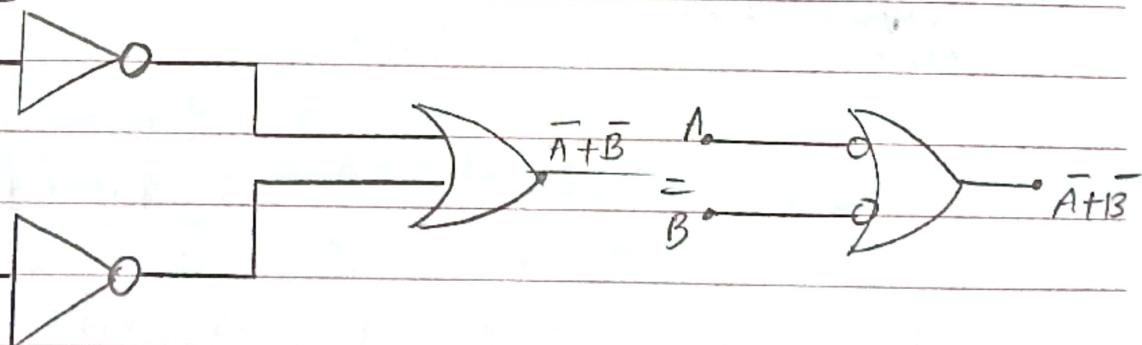

Now let us look at the truth table for this theorem:-

A	B	$A \cdot B$	$\bar{A} \cdot \bar{B}$	$A'$	$B'$	$A' + B'$
0	0	0	1	1	1	1
1	0	0	1	0	1	1
0	1	0	1	1	0	1
1	1	1	0	0	0	0

$$\bar{A} \cdot \bar{B} \leftarrow A' + \bar{B}$$

i) According to our first theorem,  
Hence it is proved that


$$A \cdot B = \bar{A} + \bar{B}$$

ii,  $\overline{A + B} = \bar{A} \cdot \bar{B}$


The complement of a logical sum equals the logical product of the complements.

### Logical Gates:-

LHS :-

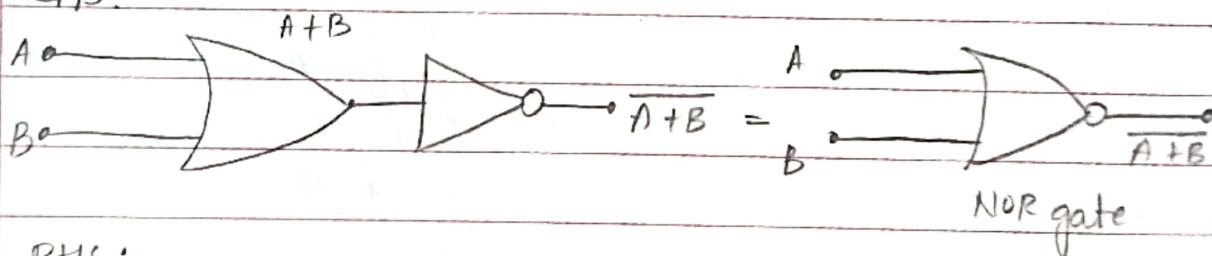

RHS :-

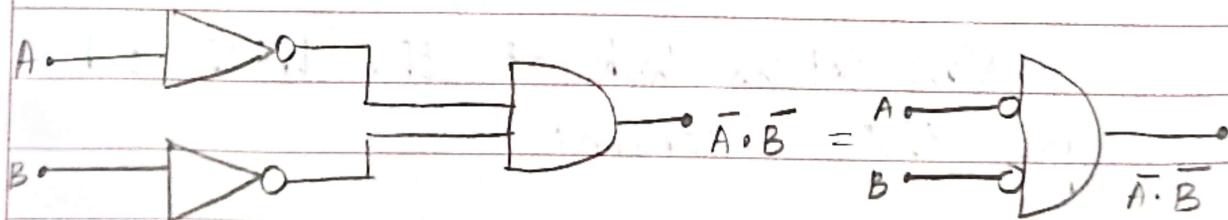

Now let us look at the truth table:-

A	B	$A'$	$B'$	$\overline{A+B}$	$\overline{A \cdot B}$	$\overline{A \cdot B}$
0	0	1	1	1	0	1
1	0	0	1	1	0	1
0	1	1	0	1	0	1
1	1	0	0	0	1	0

$\downarrow$   
 $\overline{A+B} = \overline{A \cdot B}$

$\therefore$  According to our second theorem,  
 hence it is proved that,


$$\overline{A+B} = \overline{A \cdot B}$$

③ What do you mean by full adder and full subtractor? Design a full adder using XOR gate.

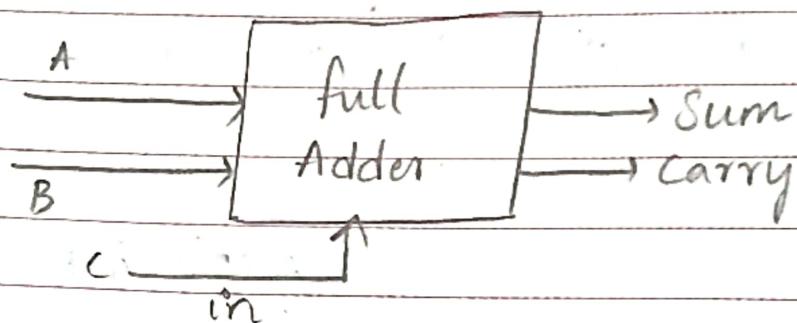(i) Full Adder:-

- To overcome the limitations faced with half Adders, full adders are implemented.
- It is a arithmetic combinational logic circuit that performs addition of three single bits.
- It contains three inputs ( $A, B, C_{in}$ ) and


- produces two outputs (sum & Cout)
- where,  $C_{in} \rightarrow$  carry in and  $C_{out} \rightarrow$  carry out
- It is designed to add, 2 single bits with carry i.e., 3 i/p's and 2 o/p's




Truth Table :-

Inputs			Outputs	
A	B	$C_{in}$	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

## K-map Simplification:-

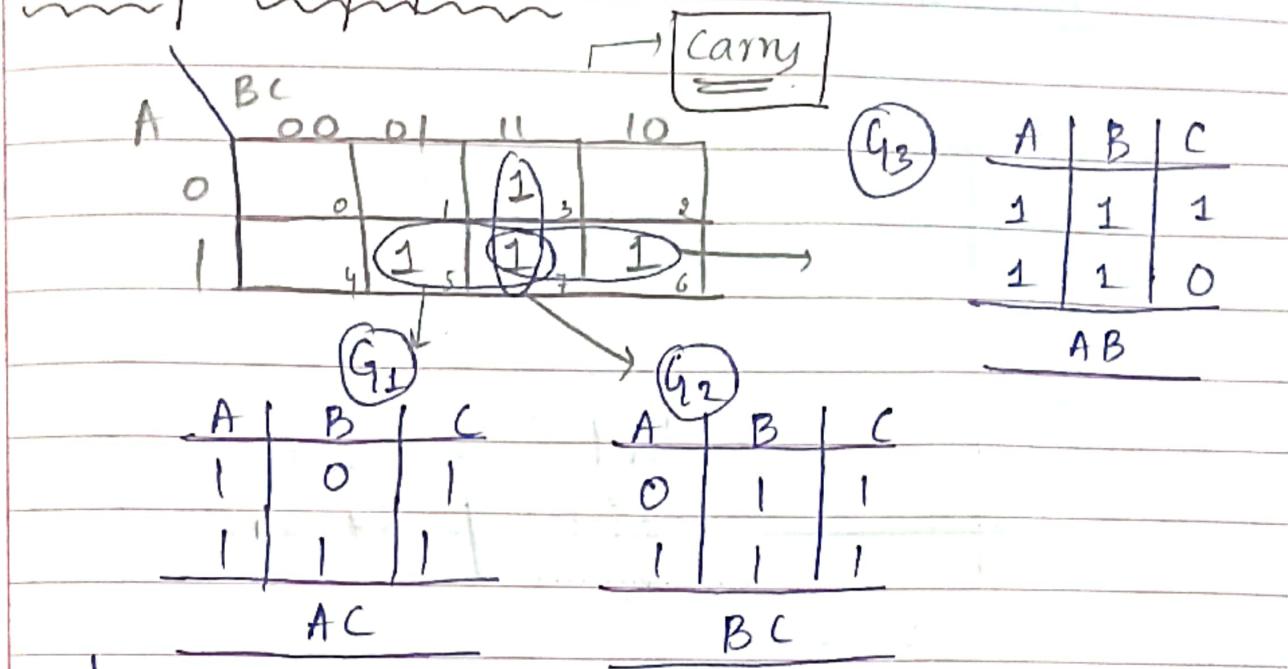

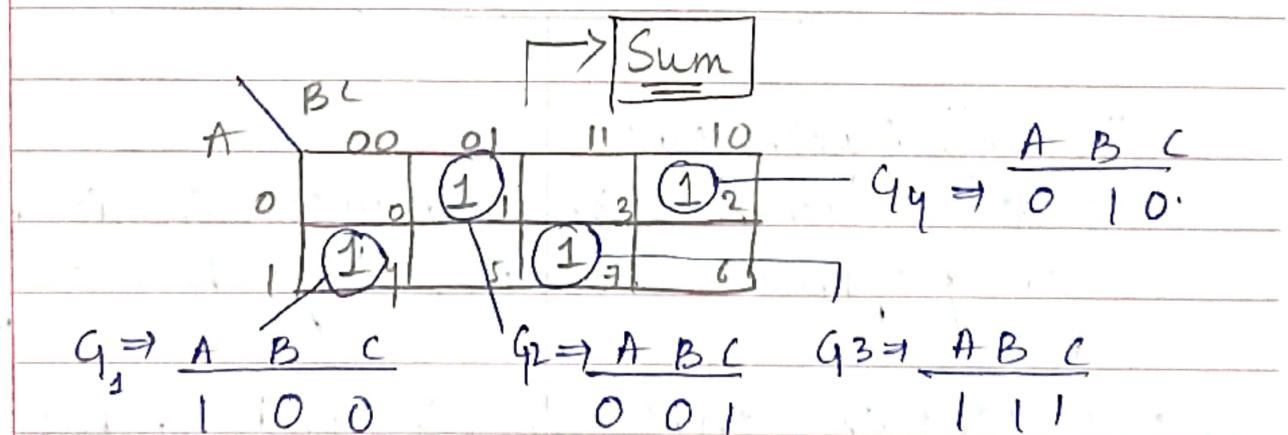
The equation obtained is  $\Rightarrow AC + BC + AB$




The equation obtained is  $\Rightarrow$

$$A'B'C + AB'C' + ABC + A'BC'$$

$\downarrow A_0 \quad \downarrow B_0$

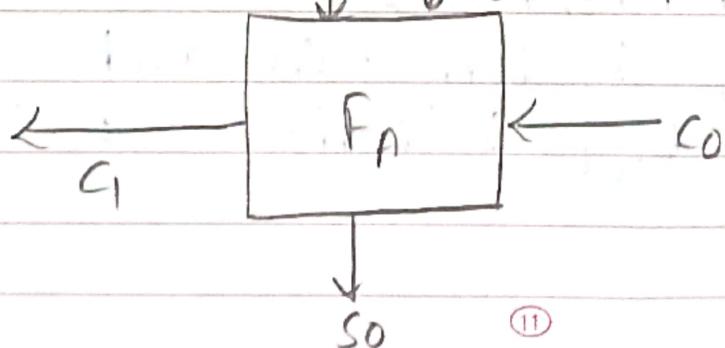


→ Full adder using XOR Gate:-

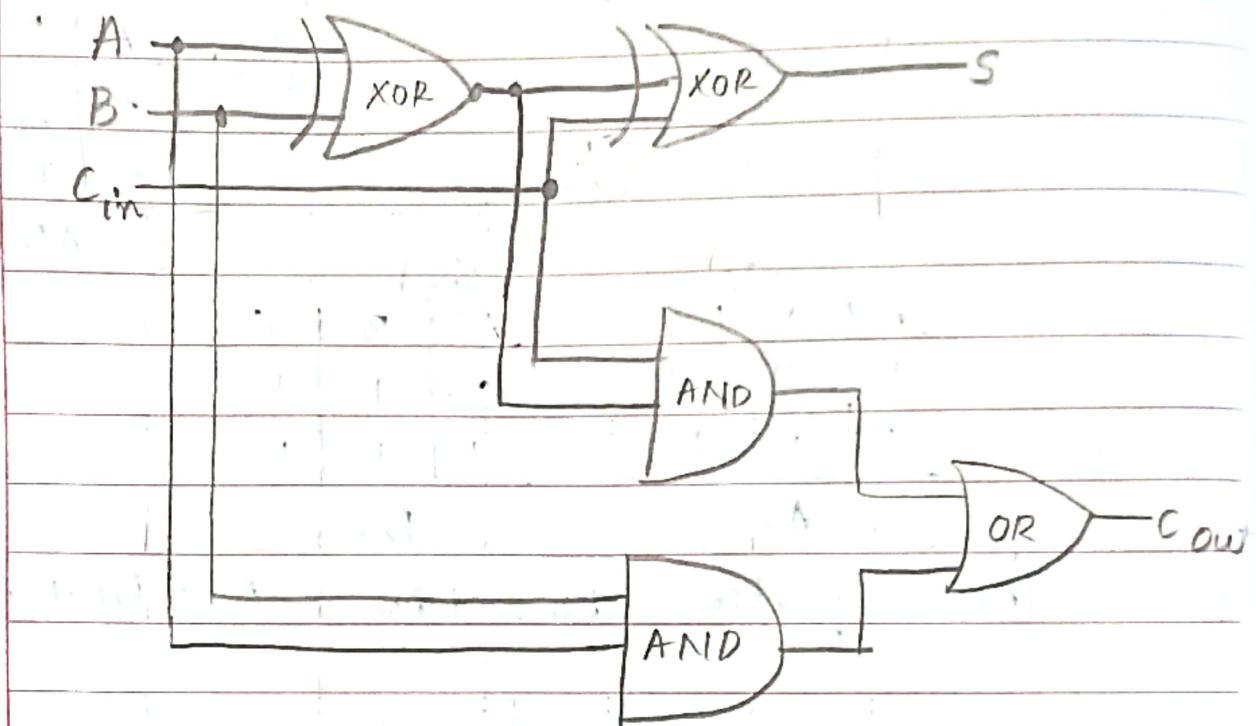

→ (iii) Full subtractor:-

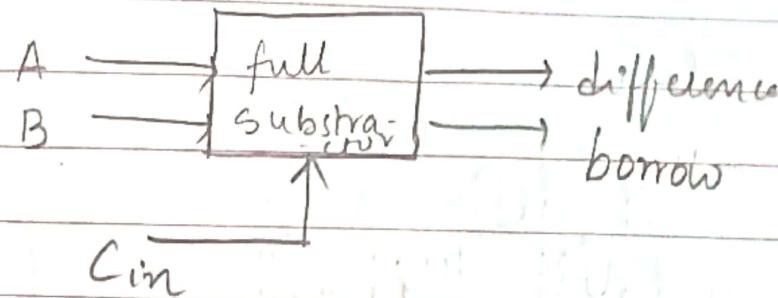
- It is a combinational logic circuit designed to perform subtraction of three single bits.
- It contains three inputs and produces two outputs.
- Where, A and B are called Minuend and Subtrahend bits.
- And C<sub>in</sub> is borrow-in and C<sub>out</sub> is borrow-out



Truth Table:-

Input			Output	
A	B	C	diff	Borrow
0	0	0	0	0
0	0	1	01	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

K-map for borrow:-

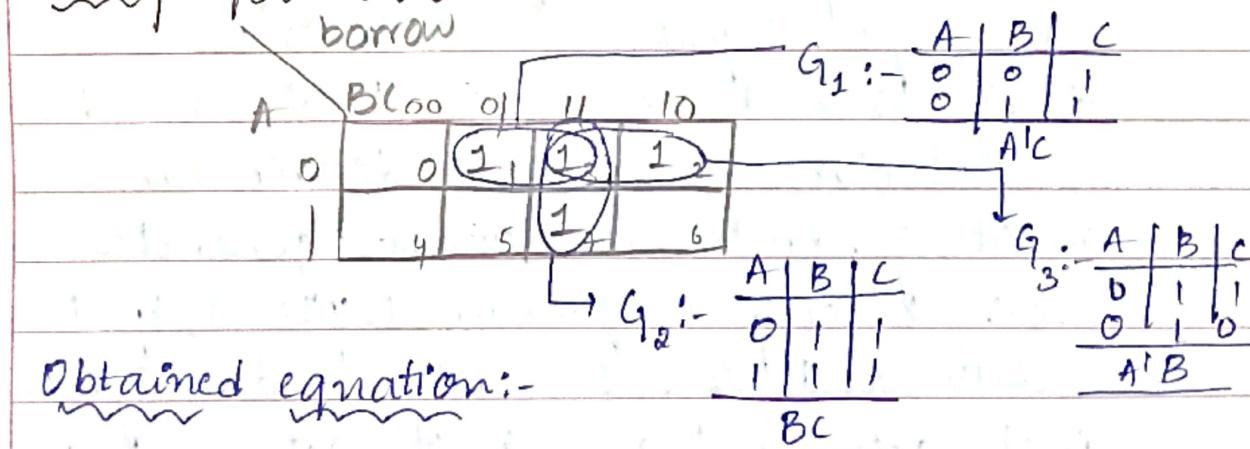

Obtained equation:-

$$A'C + BC + A'B$$

diff		BC				
A		00	01	11	10	
0		0	1	3	2	
1		4	5	7	6	

Obtained equation:-

$$= AB'C' + A'B'C + ABC + A'B'C'$$

④

Differentiate between a MUX and a DEMUX. Draw a logic circuit of  $8 \times 1$  multiplexer.

i)

Multiplexer

i, It is a combinational circuit that accepts multiple inputs of data but provides only a single input

ii, It is a data selector

iii, It generates a single output for data and signal

iv, It acts as a digital switch.

v, It performs from parallel to serial

Demultiplexer

i, It is a combinational circuit that accepts just a single input but directs it through multiple outputs

ii, It is a data distributor

iii, It generates multiple outputs for data and signal

iv, It acts as a digital circuit

v, It performs from serial to parallel

⑯

CMRIT

v; It works on an operational principle of many to one.

vii, In the process of time-division, we use a multiplexer at the end of the transmitter


viii, It behaves as a data selector because the multiplexer is an N to 1 device.

vi, It works on an operational principle of one to many.


vii, In the process of time-division, we use a demultiplexer at the end of the receiver.

viii, It behaves as a data distributor because the demultiplexer is a 1 to N device.


### Block Diagram of Multi-plexers:-

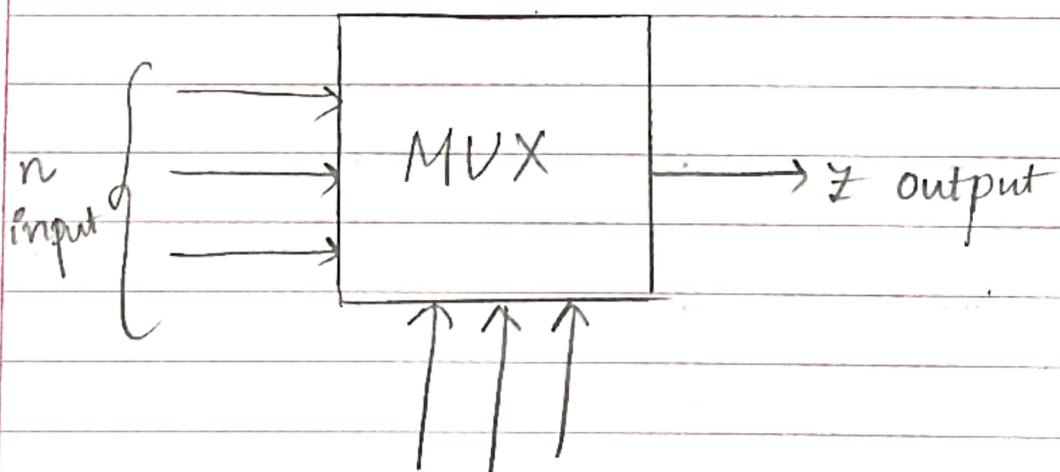

Block Diagram of Demultiplexer:-

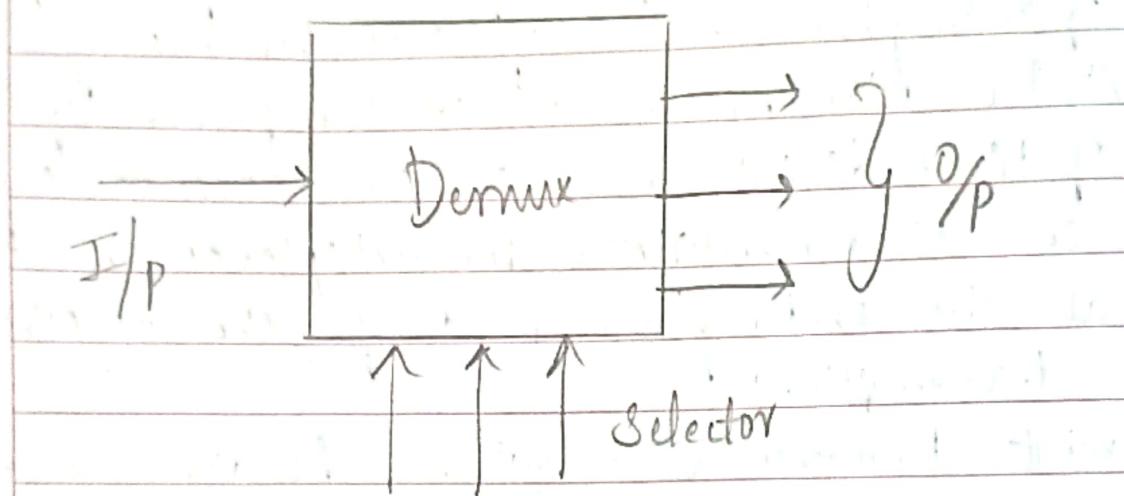

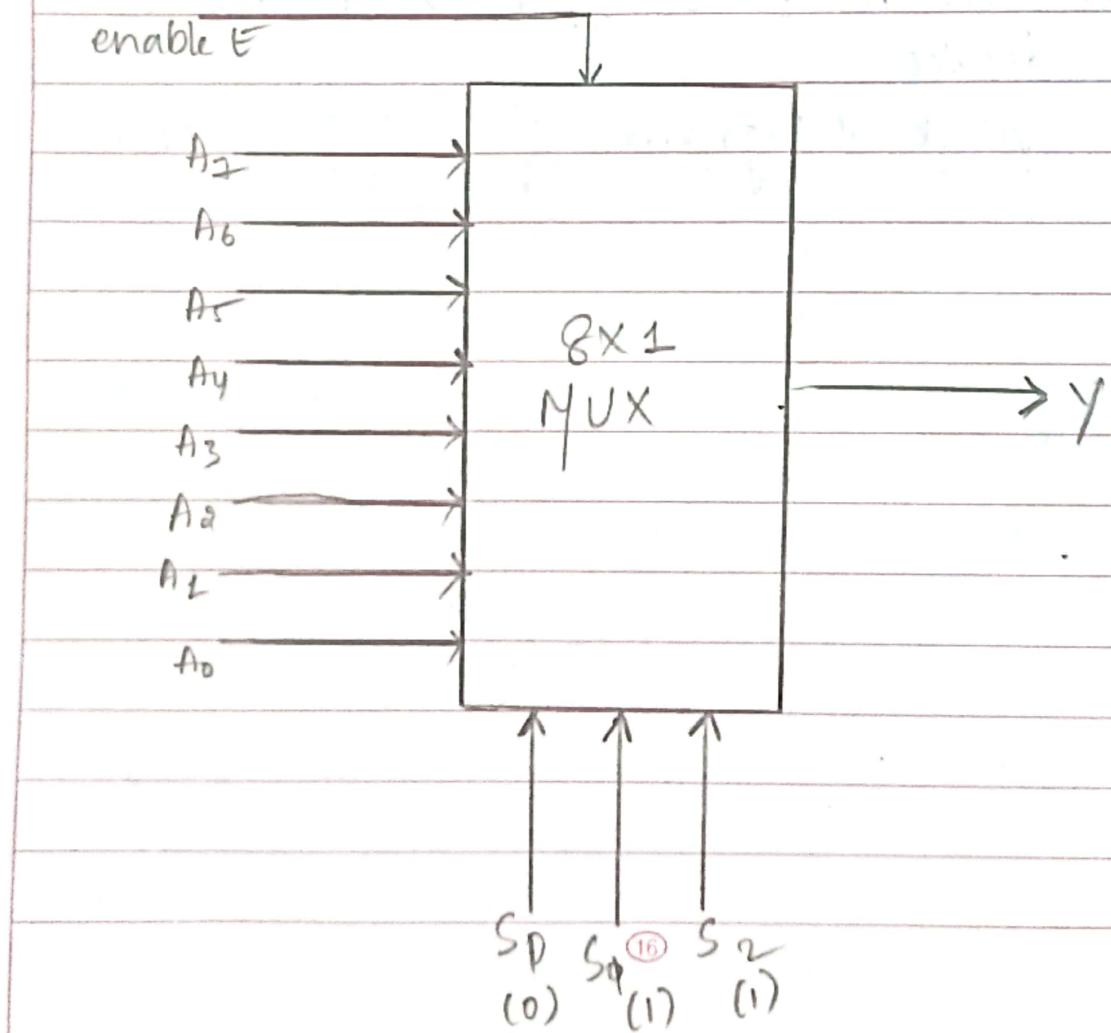(ii) logical circuit of 8\*1 multiplexer:-



Truth Table :-

Inputs			Output
$S_2$	$S_1$	$S_0$	$Y$
0	0	0	$A_0$
0	0	1	$A_1$
0	1	0	$A_2$
0	1	1	$A_3$
1	0	0	$A_4$
1	0	1	$A_5$
1	1	0	$A_6$
1	1	1	$A_7$


⑤

Discuss about Instruction Codes.

- A computer instruction is a binary code that determines the micro-operations in a sequence for a computer.
- They are saved in the memory along with the information. Each computer has its specific group of instruction.
- They can be categorized into two elements as Operation codes (opcodes) and address.

- Opcodes specify the operation for specific instructions.
- An address determines the registers or the areas that can be used for that operation.
- It consists of 12 bits of memory that are required to define the address as the memory includes 4096 words.
- The 15<sup>th</sup> bit of the instruction determines the addressing mode (where direct addressing corresponds to 0, indirect addressing corresponds to 1).

### Instruction Format :-

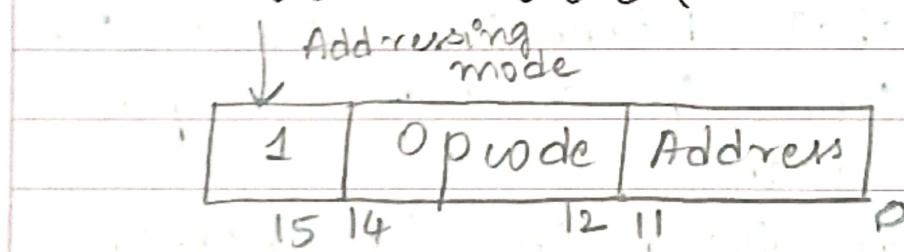

There are three parts of the instruction format as follows:-

Addressing Modes:- This field can be represented in two different ways:-

i) Direct addressing - It uses the address of the operand.

ii) Indirect addressing - It facilitates the address as a pointer to the operand.

Opcodes :- It is collection of bits that represents the basic operations including add, subtract, multiply, complement and shift. It is implemented on information that is saved in processor registers or memory.

The figure shows a diagram showing direct & indirect addresses :-

