

I - ASSIGNMENT

(Start Writing From Here)

1) Differentiate between Analog and Digital System. What are advantages of Digital System

Analog System	Digital System
* Analog signal represents physical measurements	* Digital Signals are discrete and generated by digital Modulation
* Represented by sine waves	* Represented by square waves
* Signal values can take any value within a range, providing a smooth and continuous representation	* Signal values are discrete and Quantized, allowing for precise representation and manipulation
* Prone to interference and noise, which can distort signal during transmission	* More resilient to noise due to discrete nature of signals and error correction mechanism can be employed
* Faces challenges in long distance transmission and may require amplification. Storage can be less efficient	* Allow for efficient long distances transmission and storage, with minimal signal degradation and easy replication
* Manipulating analog signal can be complex and precision may be challenging	* Enables precise manipulation, processing and analysis of data facilitating advanced computations

- | | |
|--|---|
| * Requires specialized equipment for signal processing and conditioning | * enables precise manipulation, processing and analysis of data facilitating advanced computations |
| * Multiplexing and Demultiplexing can be challenging due to the continuous nature of signals | * facilitates efficient multiplexing and demultiplexing, enhancing communication in complex systems |
| * Costs can be higher for certain applications and efficient may vary | * Often costs effective with high efficiency in data representation, transmission and processing |
| * Uses : Best suited for audio and video transmission | * Uses : Best suited for computing and digital electronics |

Advantages of Digital System

- * Reproducibility of the results and accuracy
- * ease of design : No special math skills needed to visualize the behaviour of small digital circuits
- * Flexibility and functionality
- * programmability
- * Speed : A digital logic element can produce an output in less than 10 nano seconds (10^{-8} sec)

- * Noise Immunity
- * Ease of Integration

Q) Why don't care conditions are used? Simplify $F(w, x, y, z) = \sum (1, 3, 7, 11, 15)$ which has don't care conditions are used

- ans:-
- * The don't care conditions allows us to replace the empty cell of K-map to form a grouping of variables which is larger than that of forming groups without don't care
 - * while forming groups of cells, we can consider a "Don't Care" as 1 or 0 or we can also ignore that cell
 - * A Don't care cell can be represented by cross (X) or minus (-) or phi (ϕ)
 - * To decrease min terms we use don't care $\sum (w, x, y, z) = \sum (1, 3, 7, 11, 15) + d(0, 2, 5)$

wx \ yz	00	01	11	10
00	X	1	1	X
01			1	
11			1	
10			1	

→ $w'x'$

→ yz

$$F = w'x' + yz$$

$W'Z$	$Y'Z$	00	01	11	10
00	0	1	3	2	
01	4	5	7	6	
11	12	13	15	14	
10	8	9	11	10	

- 3) Differentiate between combinational logic and Sequential logic. List some applications of Sequential logic.

Combinational Circuit	Sequential Circuit
* The output of a combinational circuit depends entirely on presents input	* The output of a sequential circuit depends on both past as well as present inputs
* It exhibits a faster speed	* It works at a comparatively slower speed
* It is comparatively easier to design	* The design of these circuits is comparatively much tougher than combinational circuit
* No feedback is present between the Input and Output	* A feedback path exists between the output and inputs

* Combinational circuit depends on time	* The circuit is time dependent
* Logic gates form the building blocks of such circuits	* Flip-flops constitute the building blocks of such a circuit
* One can make use of it for both boolean and arithmetic operations	* People mainly use them for storing data and information
* These circuits don't have a clock, they don't require triggering	* This circuit depends on a clock, it usually requires triggering
* They don't possess any memory element	* They always possess memory element
* User can feasibly use as well as handle them	* A user may not be able to handle and use these circuits easily
eg: Demultiplexer, encoder, decoder etc.	eg: Counters, Flip flops, latches

Applications of Sequential logic circuits

- * Shift registers
- * Flip flops

- * Analog to Digital and digital to Analog converters
- * Counters
- * Clocks
- * Used as Registers inside microprocessors and controllers to store temporary information
- * Data Storage

4) Describe BCD to excess-3 code conversion with truth table and logic diagram

ans: BCD digit can be controlled converted to its corresponding excess-3 code by simply adding 3 to it

The conversion of BCD to excess-3 code is performed as per following steps

step-1 : Take given BCD code

step-2 : Add $(0011)_2$ to each BCD code to obtain its equivalent excess-3 code

step-3 : Combine the excess-3 codes of each BCD code to obtain complete excess-3 code for given BCD number

(i) 0

Binary of 0 $\rightarrow 0000$

add 3 $\rightarrow 0011$

$0011 \rightarrow$ excess-3 code

(i) 1

1 → 0001

add 3 → +0011
0100

(ii) 2

→ 0010

3 → +0010
0101

(iv) 3

0011

+0011
0110

(v) 4

4 → 0100

3 → 0011
~~0111~~

(vi) 5

5 → 0101

3 → 0011
1000

(vii) 6

$$6 \rightarrow 0110$$

$$3 \rightarrow \begin{array}{r} 0011 \\ \hline 1001 \end{array}$$

(viii) 7

$$7 \rightarrow 0111$$

$$3 \rightarrow \begin{array}{r} 0011 \\ \hline 1010 \end{array}$$

(ix) 8

$$8 \rightarrow 1000$$

$$3 \rightarrow \begin{array}{r} 0011 \\ \hline 1011 \end{array}$$

(x) 9

$$9 \rightarrow 1001$$

$$3 \rightarrow \begin{array}{r} 0011 \\ \hline 1100 \end{array}$$

Truth Table

Decimal Numericals Decimal	BCD Input							
	B ₃	B ₂	B ₁	B ₀	E ₃	E ₂	E ₁	E ₀
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	0	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0

K-map for E₃ or (W)

AB \ CD				
	00	01	11	10
00	0	0	0	0
01	0	1	1	1
11	X	X	X	X
10	1	1	X	X

$$E_3 \text{ (or) } W = A + BC + BD \text{ (or) } B_3 + B_2 (B_1 + B_0)$$

K-map for E_2 (or) X :

AB \ CD	00	01	11	10
00	0	1	1	1
01	1	0	0	0
11	X	X	X	X
10	0	1	X	X

Groupings: $\overline{B}C$ (top row, columns 01, 11, 10), $B\overline{C}\overline{D}$ (column 00, rows 01, 11), $\overline{B}D$ (column 10, rows 00, 10).

$$E_2 \text{ (or) } X = B\overline{C}\overline{D} + \overline{B}C + \overline{B}D$$

K-map for E_1 (or) Y :

AB \ CD	00	01	11	10
00	1	0	1	0
01	1	0	1	0
11	X	X	X	X
10	1	0	X	X

Groupings: $\overline{C}\overline{D}$ (column 00, rows 00, 01, 10), CD (column 11, rows 00, 01, 10).

$$E_1 \text{ (or) } Y = \overline{C}\overline{D} + CD$$


K-map for E_0 (or) Z :

AB \ CD	00	01	11	10
00	1	0	0	1
01	1	0	0	1
11	X	X	X	X
10	1	0	X	X

Groupings: $\overline{C}\overline{D}$ (column 00, rows 00, 01, 10), $C\overline{D}$ (column 10, rows 00, 01, 10).


$$E_0 \text{ (or) } Z = \overline{C}\overline{D} + C\overline{D}$$

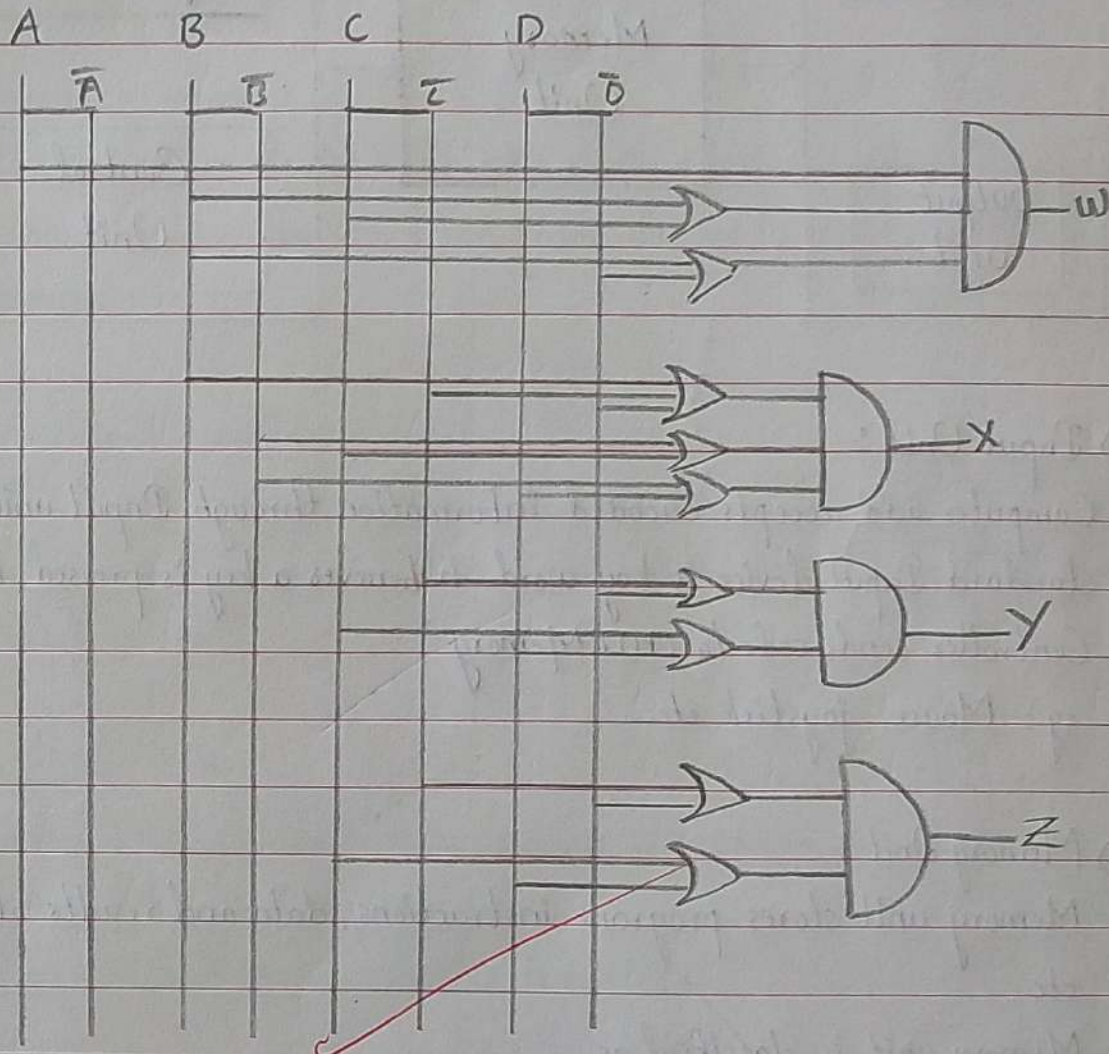BCD to excess-3 code converter logic diagram :



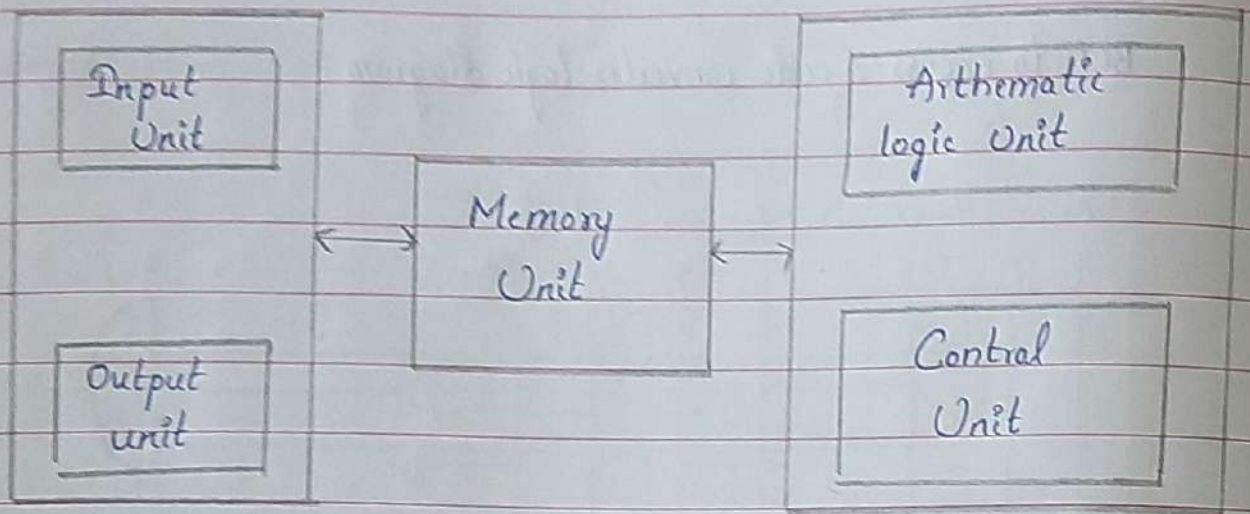5) Explain about functional units of basic computer

ans: Functional unit : A computer in its simplest form compress five functional units namely input unit, out put unit, memory unit, Arthematic and logical unit and control unit



1) Input Unit :-

Computer add accepts encoded information through Input unit. The standard Input device is key word. Whenever a key is pressed, keyboard, Controller sends code to CPU/Memory
eg:- Mouse, joystick etc...

2) Memory Unit :-

Memory unit stores program instructions, data and results of computations etc...

Memory unit is classified as

- i) Primary/Main Memory
- ii) Secondary/Auxiliary Memory

Primary memory

* ROM (Read Only Memory) holds system programs and firm ware routines such as BIOS, POST

* RAM (Random Access Memory) is termed as write/read memory or user memory that holds runtime program Instructions and data

Secondary memory

* It is a storage device that CPU can't access directly. It is a permanent storage device. The CPU access these devices through out input/output channel

3) Arithmetic and Logic Unit

ALU Consists of necessary logic circuits like adder, comparators etc., to perform operations of addition, subtraction, multiplication, comparison of 2 numbers etc.

4) Output Unit

Computer after computation returns the computed results, error message etc, via output unit

The standard output devices is a video

5) Control Unit

Control unit co-ordinates activities of all units by issuing control signals. Control signals issued by control unit govern the data transfers and then appropriate operations takes place